

CHAPTER XII

SINGLE CYCLE DATAPATH UNIT


READ SINGLE CYCLE DATAPATH FREE-DOC ON COURSE WEBPAGE

- From the previous chapter, we now have a number of datapath elements such as
 - Register file (**RF**)
 - Adder/subtractor unit (**AU**)
 - Logical unit (**LU**)
 - Shift unit (**SU**)
- The question now is how to take these datapath elements and form a **datapath unit** (DPU).
- The DPU that we will focus on in this chapter is a basic single cycle DPU using a *triple bus internal architecture*.

SINGLE CYCLE DPU

DATAPATH ELEMENTS

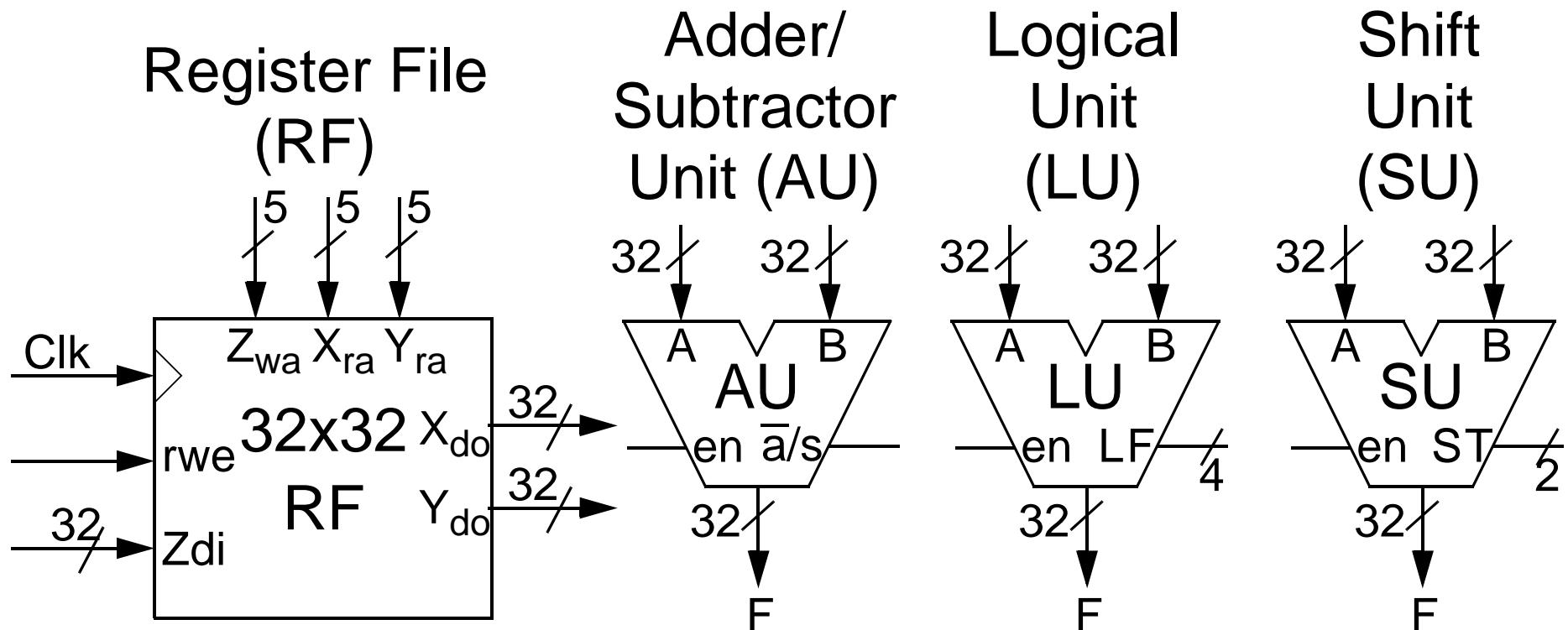- For our examples, we will use the following 32-bit type DPU elements.




- These allow us to design a 32-bit word computer with 32 registers.
- Of course, other word sizes could be used for other designs.

SINGLE CYCLE DPU

ADD/SUBTRACT MACHINE

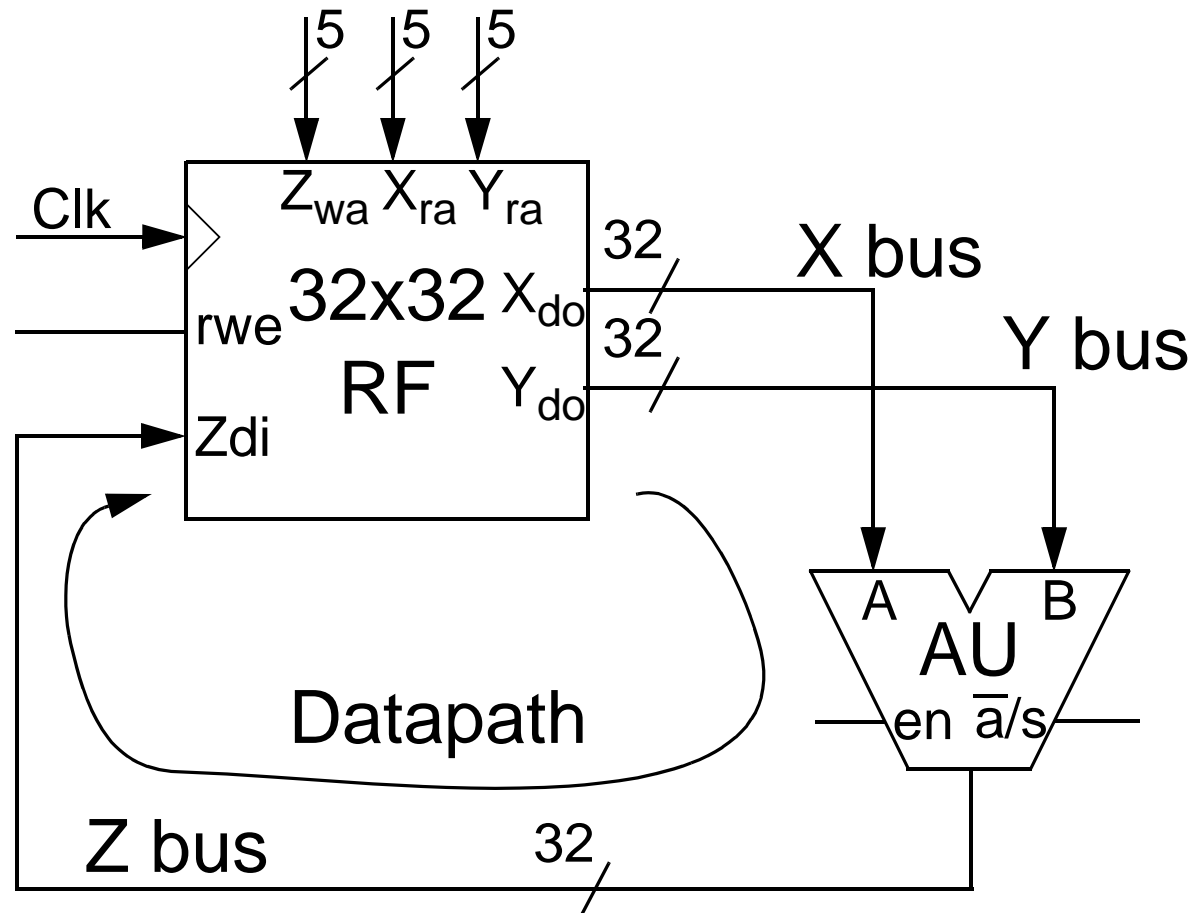- Below is a simple datapath with a register file and adder/subtractor.



Important:

It only takes 1 clock cycle to add/subtract and store the result.

- This structure is also known as a **triple bus internal DPU architecture**.

SINGLE CYCLE CPU

ADD/SUBTRACT MACHINE

- This simple add/subtract machine DPU allows us to add or subtract values in our registers and store the result back into another register.
- For instance, say that we wanted to **add** the contents of register **R1** with register **R2** and store the result back in register **R3**.

$$\mathbf{R3} = \mathbf{R1} + \mathbf{R2}$$

- What control signals are required?
 - $\bar{a}/s = 0$ and $en = 1$ for **AU**.
 - $X_{ra} = 00001$, $Y_{ra} = 00010$, $Z_{wa} = 00011$, and $rwe = 1$ for **RF**.
- These control signals are applied at the beginning of a clock cycle. The signals then propagate forming the sum at the output of the **AU**. At the end of the clock cycle, the sum (on **Z bus**) is clocked into **R3**.

SINGLE CYCLE CPU

ADD/SUBTRACT MACHINE

- What if instead we wanted to perform the following operation.


$$\mathbf{R2 = R1 + R2}$$

- The control signals required are
 - $\bar{a}/s = 0$ and $en = 1$ for **AU**.
 - $X_{ra} = 00001$, $Y_{ra} = 00010$, $Z_{wa} = 00010$, and $rwe = 1$ for **RF**.
- What is the result of this if the current value of **R1=0x00000001** and **R2=0x00000003**?
 - The register **R2** would be updated at the end of the clock cycle with the value **0x00000004**.
- Remember, the current value of **R2** is put on the **X** or **Y bus**, and it is only at the **END** of the clock cycle that the contents of **R2** get changed.

SINGLE CYCLE DPU

BASIC SINGLE CYCLE DPU

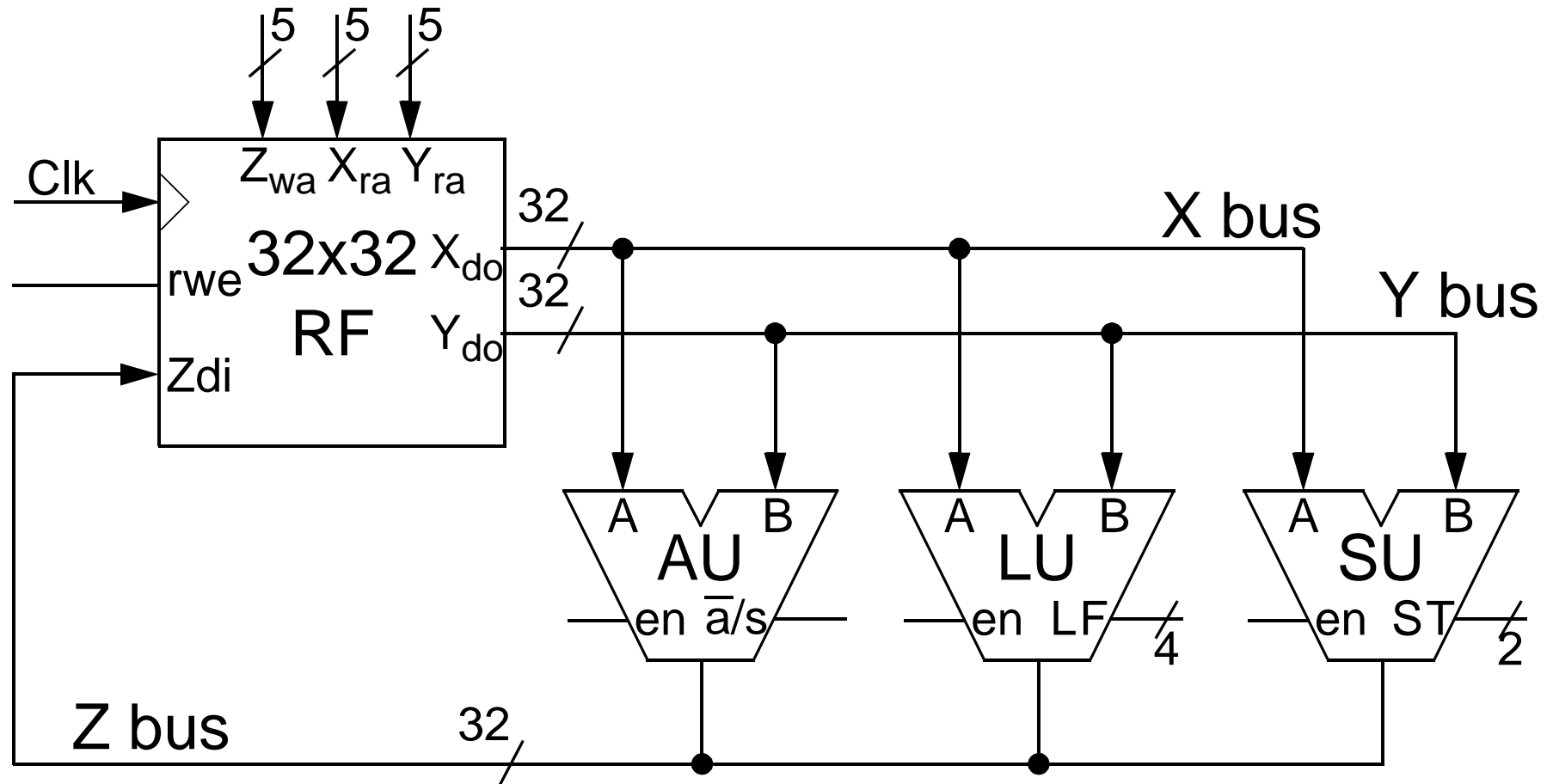- A more useful single cycle datapath can be as follows.



- This structure is still a **triple bus internal DPU architecture**.

- How does this change the additions we were doing earlier?
- Say we want to again perform the following addition.

$$R3 = R1 + R2$$


- The control signals we would need are
 - $\bar{a}/s = 0$ and $en = 1$ for **AU**.
 - $en = 0$ for **LU**.
 - $en = 0$ for **SU**.
 - $X_{ra} = 00001$, $Y_{ra} = 00010$, $Z_{wa} = 00011$, and $rwe = 1$ for **RF**.
- Notice that we use the same control signals as before, but now include signals to disable the **LU** and **SU** during this addition clock cycle.

- Another operation we might want to do with this DPU is perform a logical shift of the contents of **R15** by a distance indicated in **R6**.
- The control signals required are
 - **en = 0** for **AU**.
 - **en = 0** for **LU**.
 - **en = 1** and **ST = 00** for **SU**.
 - **X_{ra} = 01111**, **Y_{ra} = 00110**, **Z_{wa} = 01111**, and **rwe = 1** for **RF**.
- Notice that this set of control signals disables the **AU** and **LU** while enabling the **SU**.
- The **SU** is set to do a logical shift with **ST = 00**.
- The distance of the shift is according to what is in **R6**.
- The result is stored back in **R15** with **Z_{wa} = 01111** and **rwe = 1** for **RF**.

SINGLE CYCLE DPU

ARITHMETIC LOGIC UNIT

 
- Since only one of **AU**, **SU**, or **LU** will be active at a time in this architecture, we will combine to form an **arithmetic logic unit (ALU)**.



SINGLE CYCLE DPU

SINGLE CYCLE DPU W/ALU

 - Using our **ALU**, the DPU can be redrawn as follows.




- This structure is still a **triple bus internal DPU architecture**.

SINGLE CYCLE DPU

IMMEDIATE REGISTER

 - Many designs also include some form of immediate register.



- Allows for operations such as **R28 = R5 + Immediate**.

SINGLE CYCLE DPU

IMMEDIATE REGISTER


- The **im_en** line does two things:
 - When **0**, **im_en** controls
 - **immediate register outputs** to go to **high impedance** so as **NOT** to affect **Y bus**.
 - **register file Y data out** to output corresponding register value.
 - When **1**, **im_en** controls
 - **immediate register** to output register value to **Y bus**.
 - **register file Y data out** to go to **high impedance** so as **NOT** to affect **Y bus**.
- The **im_va** lines pass a value to the immediate register.

SINGLE CYCLE DPU

INCLUDING MEMORY

- SINGLE CYCLE DPU
- ARITHMETIC LOGIC UNIT
- SINGLE CYCLE DPU W/ALU
- IMMEDIATE REGISTER

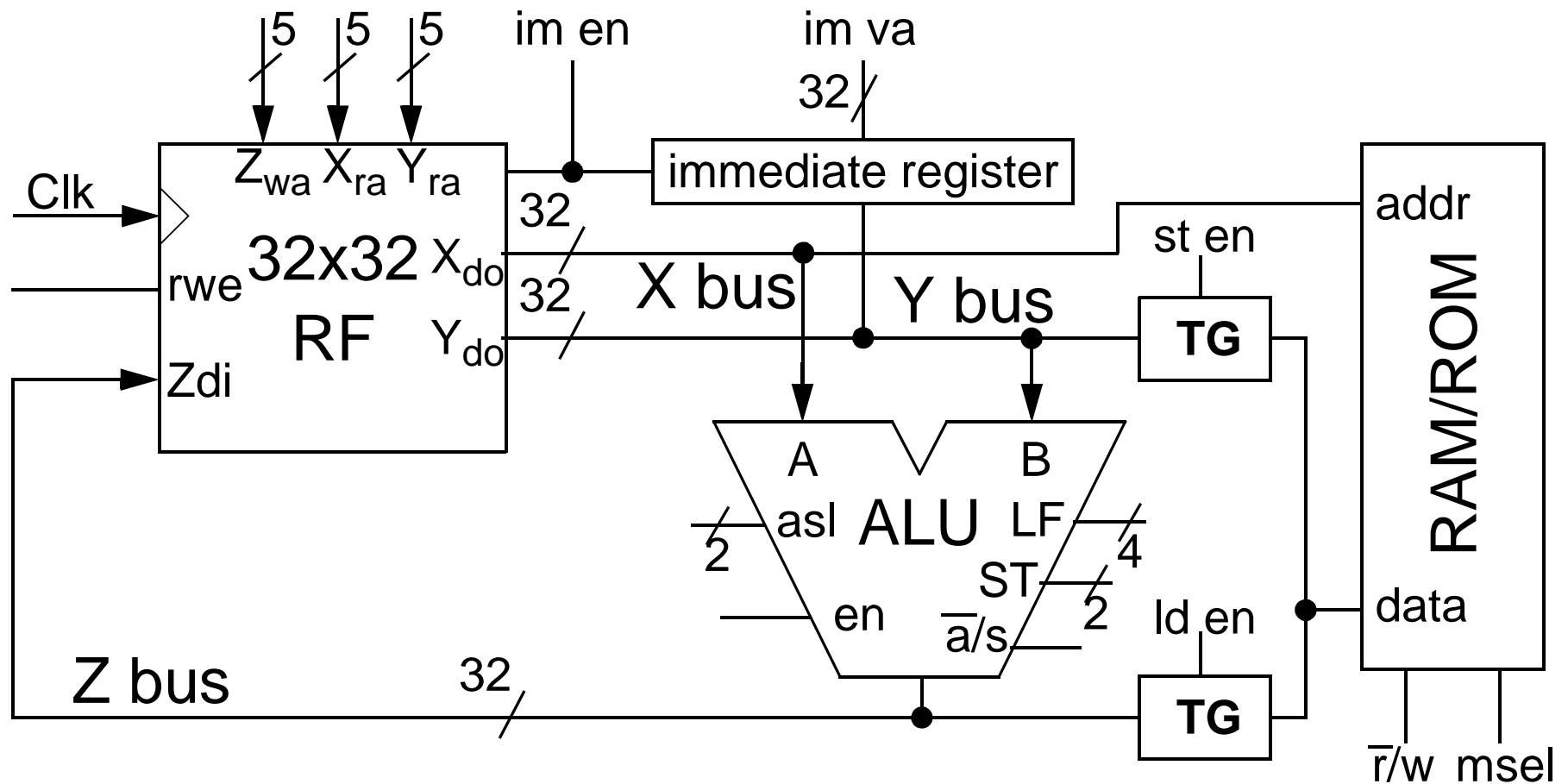- 32x32 bits is not sufficient memory for most computers.
- We can include external memory (SRAM, DRAM, etc.) as follows.



SINGLE CYCLE DPU

INCLUDING MEMORY

- The included has the following characteristics
 - 32 address lines
 - 32 data lines
 - a read/write line
 - a chip select or memory select line
- Two transmission gates block the bidirectional data lines for the memory.
 - Notice that if **st_en** is high, then we can potentially write to the memory.
 - Notice that if **ld_en** is high, then we can potentially read from the memory.

SINGLE CYCLE DPU

READING FROM MEMORY

- We wish to be able to read and write from our memory.
- A sample read/load operation can be expressed as follows

$$\mathbf{R4 = M[R7]}$$

- This operation uses the value in **R7** as the address to the memory and reads the value at that address in the memory to **R4**.
- What control signals are required?
 - **en = 0** for **ALU**.
 - **X_{ra} = 00111**, **Y_{ra} = XXXXX**, **Z_{wa} = 00100**, and **rwe = 1** for **RF**.
 - **st_en = 0** and **ld_en = 1**
 - **~r/w = r** and **msel = 1**

SINGLE CYCLE DPU

WRITING TO MEMORY

- A sample write/store operation can be expressed as follows

$$\mathbf{M[R5] = R9}$$

- This operation uses the value in **R5** as the address to the memory and write the value in **R9** to that address in the memory.
- What control signals are required?
 - **en = 0** for **ALU**.
 - **X_{ra} = 00101**, **Y_{ra} = 01001**, **Z_{wa} = XXXXX**, and **rwe = 0** for **RF**.
 - **st_en = 1** and **ld_en = 0**
 - **~r/w = w** and **msel = 1**

SINGLE CYCLE DPU

MICROCODE

- Microcode in a processor are all of the control signals required to execute an operation for a clock cycle.
- We have actually looked at examples of a microcode operation when we considered various operations such as

$$\mathbf{R3 = R1 + R2}$$

or

$$\mathbf{M[R5] = R9}$$

- Later we will talk about macrocode which are longer operations consisting of many microcode operation over a number of clock cycles.