

CHAPTER VI



COMBINATIONAL LOGIC BUILDING BLOCKS

- Combinational logic
 - Output at any time is determined completely by the current input.
 - We will later consider circuits where the output is determined by the input and the current state (memory) of the system.
 - In this chapter we will consider some useful building blocks that can be pieced together and used in larger designs. This will include:
 - Multiplexers (selectors) and demultiplexers (distributors)
 - Encoders, priority encoders, decoders
 - Adders (full and half)
 - Parity generators and parity checkers
 - Shifters and rotators
 - Comparators

DECODERS

BASIC DECODER

  - Standard decoder is an n -to- m -line decoder, where $m \leq 2^n$.
- Example: 3-to-8-line decoder




- All outputs D_m are low except for the one corresponding to the binary value of the input $A_n \dots A_1 A_0$.

DECODERS

DECODERS WITH ENABLE

- Often, combinational logic building blocks will also have an enable line that turns on outputs or leaves them off.

3-to-8 Decoder
with Enable

 

DECODERS

TRUTH TABLES



- Truth table for a **3-to-8-line decoder**:

Inputs				Outputs							
A ₂	A ₁	A ₀	E	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
X	X	X	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	0	0	0	1	0
0	1	0	1	0	0	0	0	0	1	0	0
0	1	1	1	0	0	0	0	1	0	0	0
1	0	0	1	0	0	0	1	0	0	0	0
1	0	1	1	0	0	1	0	0	0	0	0
1	1	0	1	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

DECODERS

IMPLEMENTATION

  - How can a decoder be implemented? Fill in the circuit!




DECODERS

DESIGNING WITH DECODERS

- Any Boolean function can implemented using a **decoder** and **OR** gates by ORing together the function's **minterms**.

Inputs			Outputs	
A_2	A_1	A_0	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

 

DECODERS


DECODER NETWORKS

- We can also use multiple decoders to form a larger decoder.

3-to-8 Decoder Implemented
with two 2-to-4 Decoders

A₂ used with enable input
to control which decoder
will output the **1**.

 
A₁ and **A₀** used to select
which output on specific
decoder will output **1**.




ENCODERS

BASIC ENCODER

 - Standard binary encoder is an m -to- n -line encoder, where $m \leq 2^n$.
- Example: 8-to-3-line encoder



Example:
Input of 00010000

 

ENCODERS

ENCODER TRUTH TABLE

- Truth table for an **8-to-3-line encoder**:

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1


- Assumed that only one input is **1**. What happens if more than one is **1**?

ENCODERS

DESIGNING WITH ENCODERS

- Encoders are useful when the occurrence of one of several disjoint events needs to be represented by an integer identifying the event.

Example: Wind direction encoder

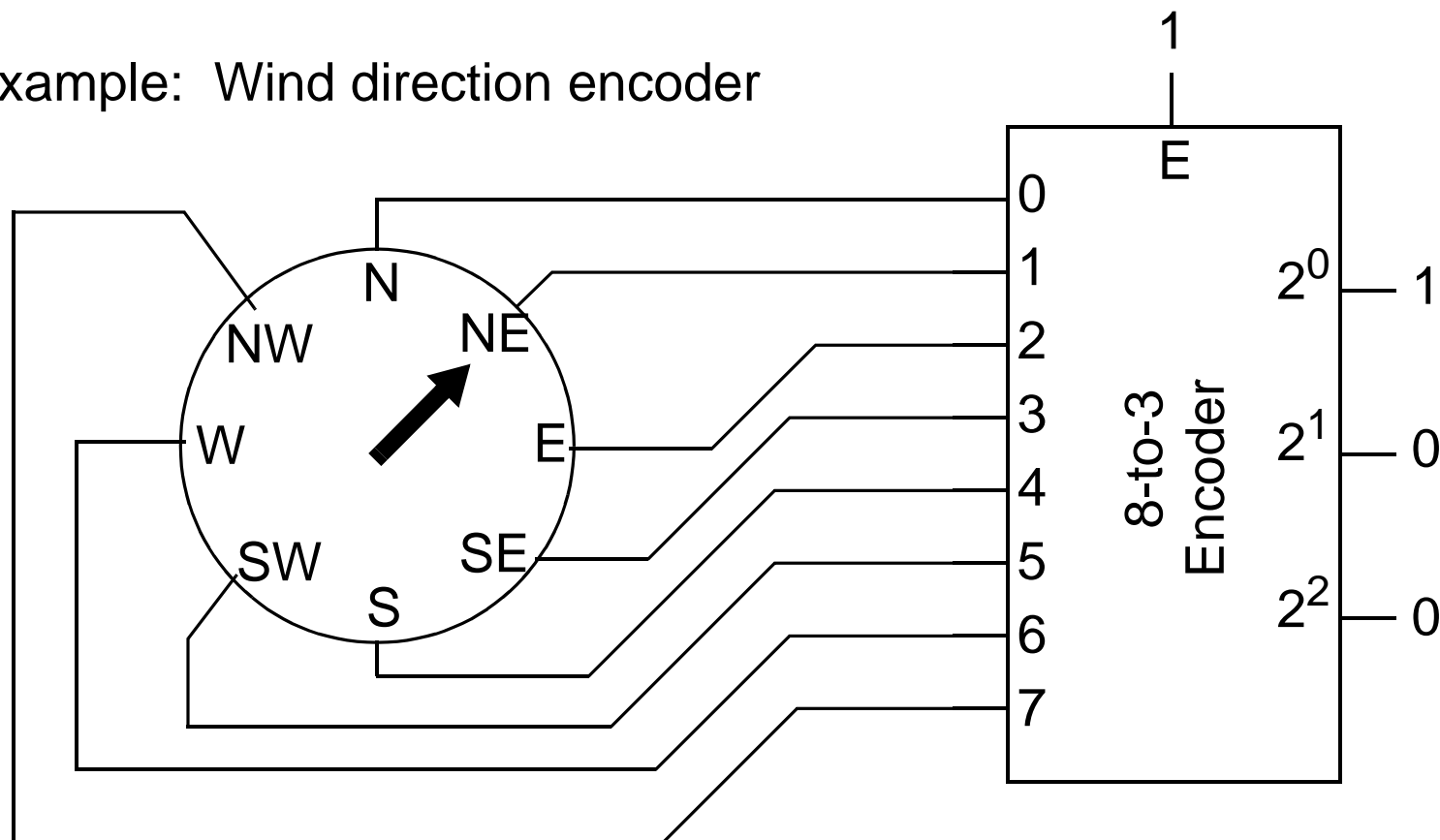

pp. 253-254 of Ercegovic, Lang and Moreno, "Introduction to Digital Systems", 1999.

ENCODERS

PRIORITY ENCODERS

- A priority encoder takes the input of 1 with the highest index and translates that index to the output.


Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

ENCODERS

DESIGN WITH P-ENCODER

- Priority encoders are useful when inputs have a predefined priority and we wish to select the input with the highest priority.

Example: Resolving interrupt requests

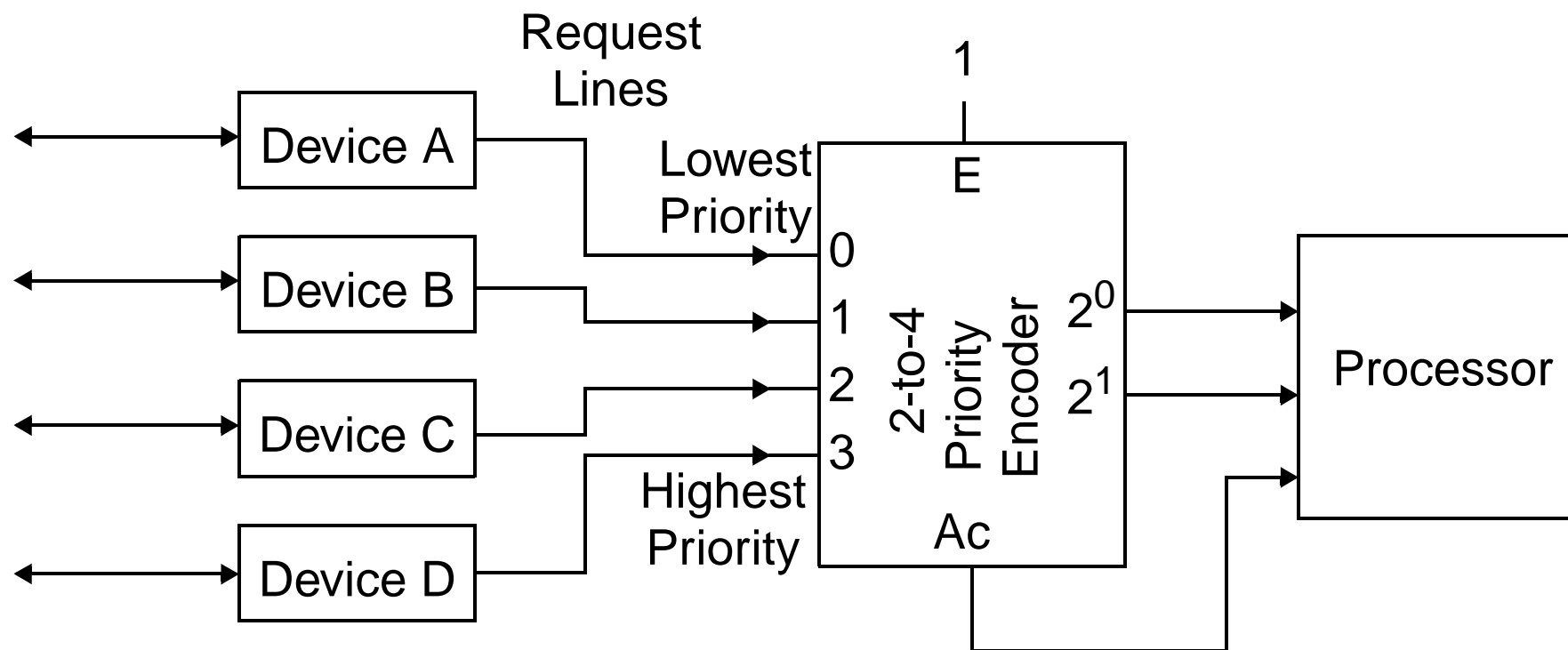


pp. 253-256 of Ercegovac, Lang and Moreno, "Introduction to Digital Systems", 1999.

MULTIPLEXERS

BASIC MULTIPLEXER (MUX)

 - Selects one of many inputs to be directed to an output.




		Inputs				Output
X	Y	A ₃	A ₂	A ₁	A ₀	F
0	0	X	X	X	0	A ₀ =0
0	1	X	X	0	X	A ₁ =0
1	0	X	0	X	X	A ₂ =0
1	1	0	X	X	X	A ₃ =0
0	0	X	X	X	1	A ₀ =1
0	1	X	X	1	X	A ₁ =1
1	0	X	1	X	X	A ₂ =1
1	1	1	X	X	X	A ₃ =1

MULTIPLEXERS

USING PASS GATES

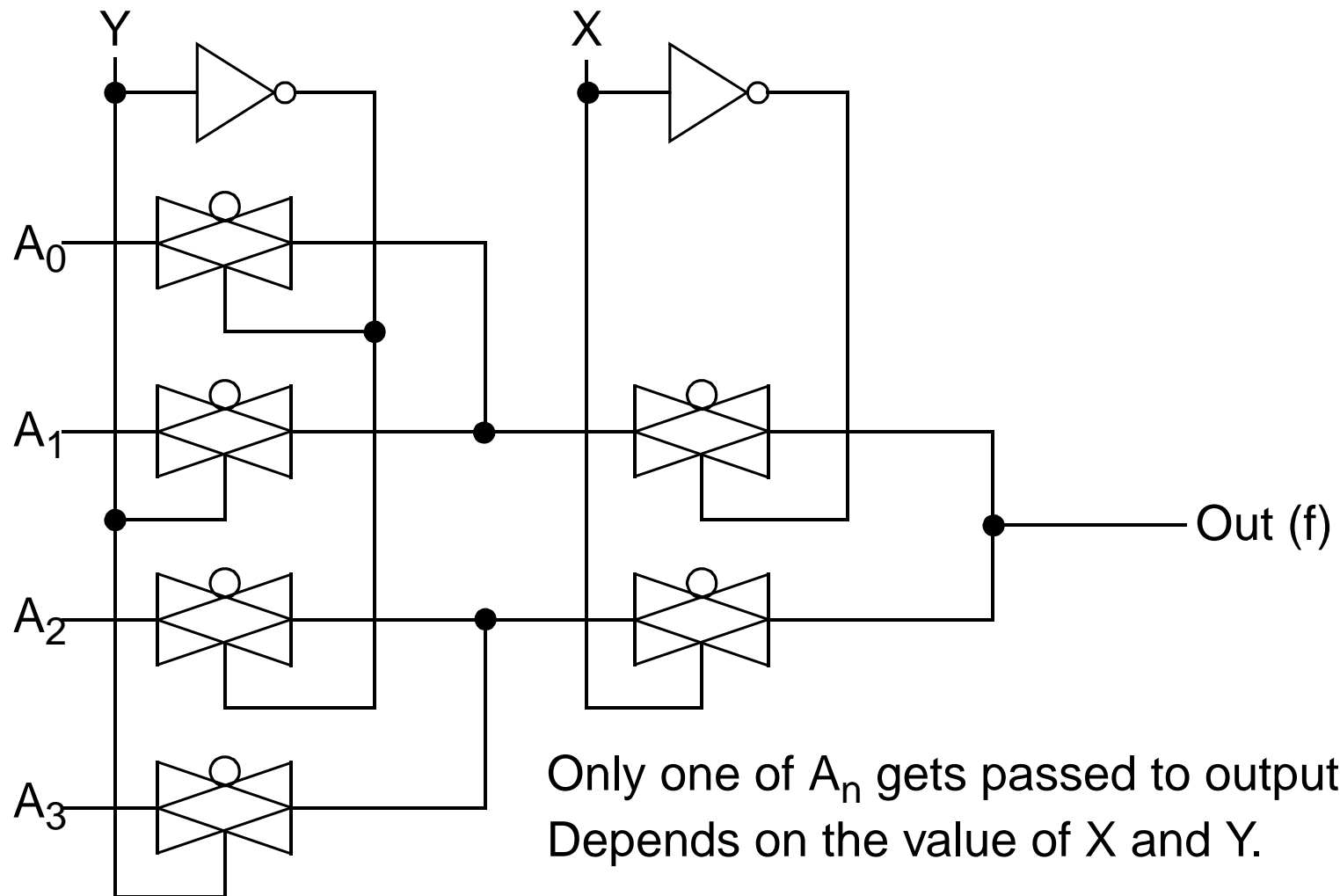- The **4x1 mux** can be implemented with **pass gates** as follows.




MULTIPLEXERS

DESIGN WITH MULTIPLEXERS

- ENCODERS
- MULTIPLEXERS
 - BASIC MULTIPLEXER
 - USING PASS GATES

- Any Boolean function can be implemented by setting the inputs corresponding to the function and the selectors as the variables.


Example:

 

DEMULTIPLEXERS

BASIC DEMULTIPLEXER

 - Takes one input and selects one of many outputs to direct the input.




Inputs			Outputs			
X	Y	W	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	W=0
0	1	0	0	0	W=0	0
1	0	0	0	W=0	0	0
1	1	0	W=0	0	0	0
0	0	1	0	0	0	W=1
0	1	1	0	0	W=1	0
1	0	1	0	W=1	0	0
1	1	1	W=1	0	0	0

DEMULTIPLEXERS

DESIGN W/ DEMULTIPLEXERS

- A demultiplexer is useful for routing an input to a desired location.


Example:

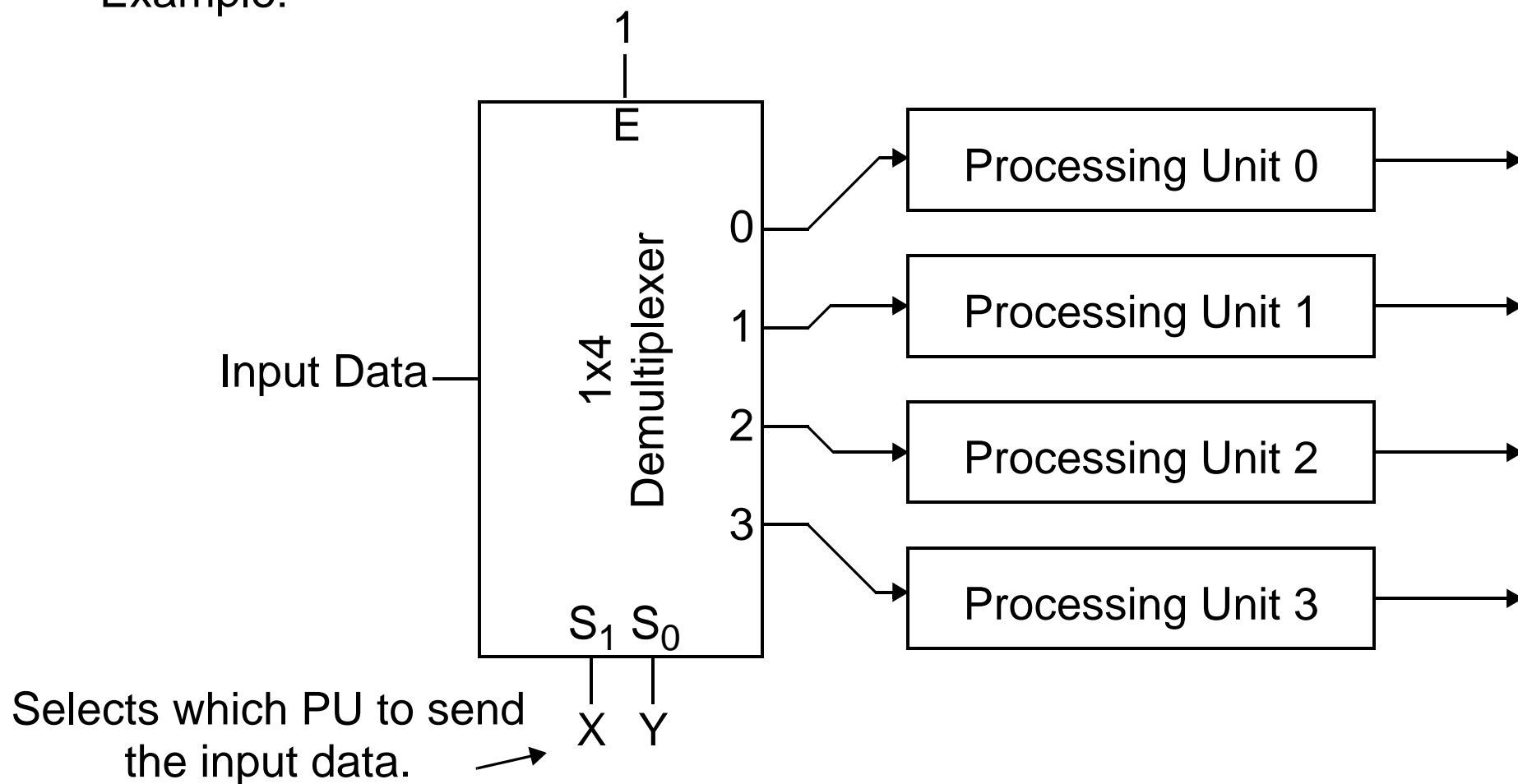


ADDERS

HALF- AND FULL-ADDERS

 - Two basic building blocks for arithmetic are half- and full-adders as depicted by the block diagrams below.



Half-adder

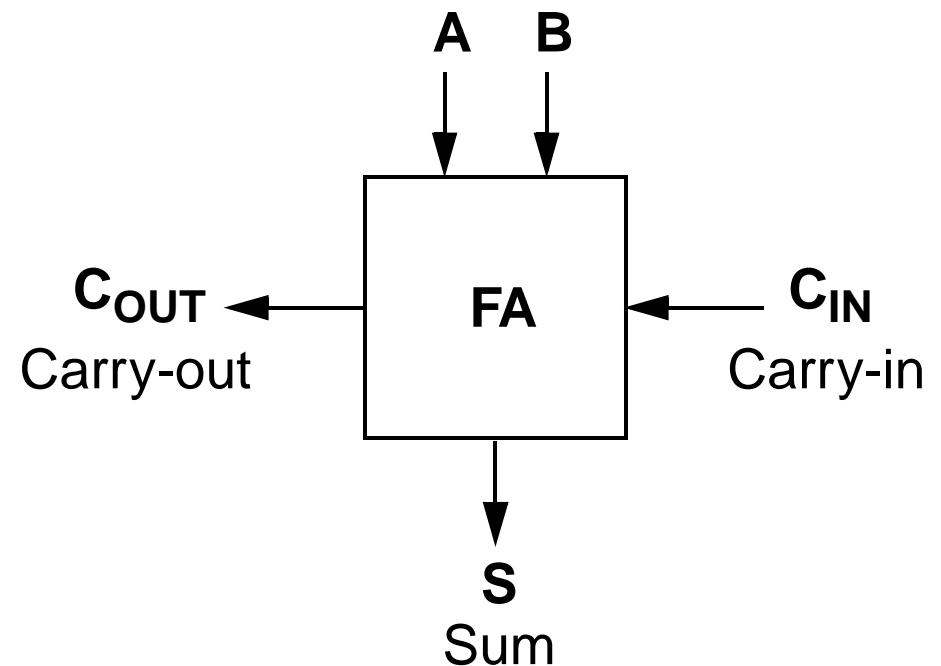

Full-adder

ADDERS


HALF-ADDER (HA)

- First of all, how do we add?
- 2's complement arithmetic allows us to add numbers normally.

Inputs		Sum	Carry-out
A	B	S	C _{OUT}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C_{OUT} = AB$$

 

ADDERS

FULL-ADDER (FA) (1)

- Half-adder missed a possible carry-in. A full-adder (FA) includes this additional carry-in.

Inputs		Carry-in	Sum	Carry-out
A	B	C _{IN}	S	C _{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = AB + C_{IN}(A \oplus B)$$


ADDERS

FULL-ADDER (FA) (2)

- ADDERS
 - HALF- & FULL-ADDERS
 - HALF-ADDER (HA)
 - FULL-ADDER (FA)

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = AB + C_{IN}(A \oplus B)$$

 


ADDERS

BINARY ADDITION

- ADDERS
 - HALF- & FULL-ADDERS
 - HALF-ADDER (HA)
 - FULL-ADDER (FA)

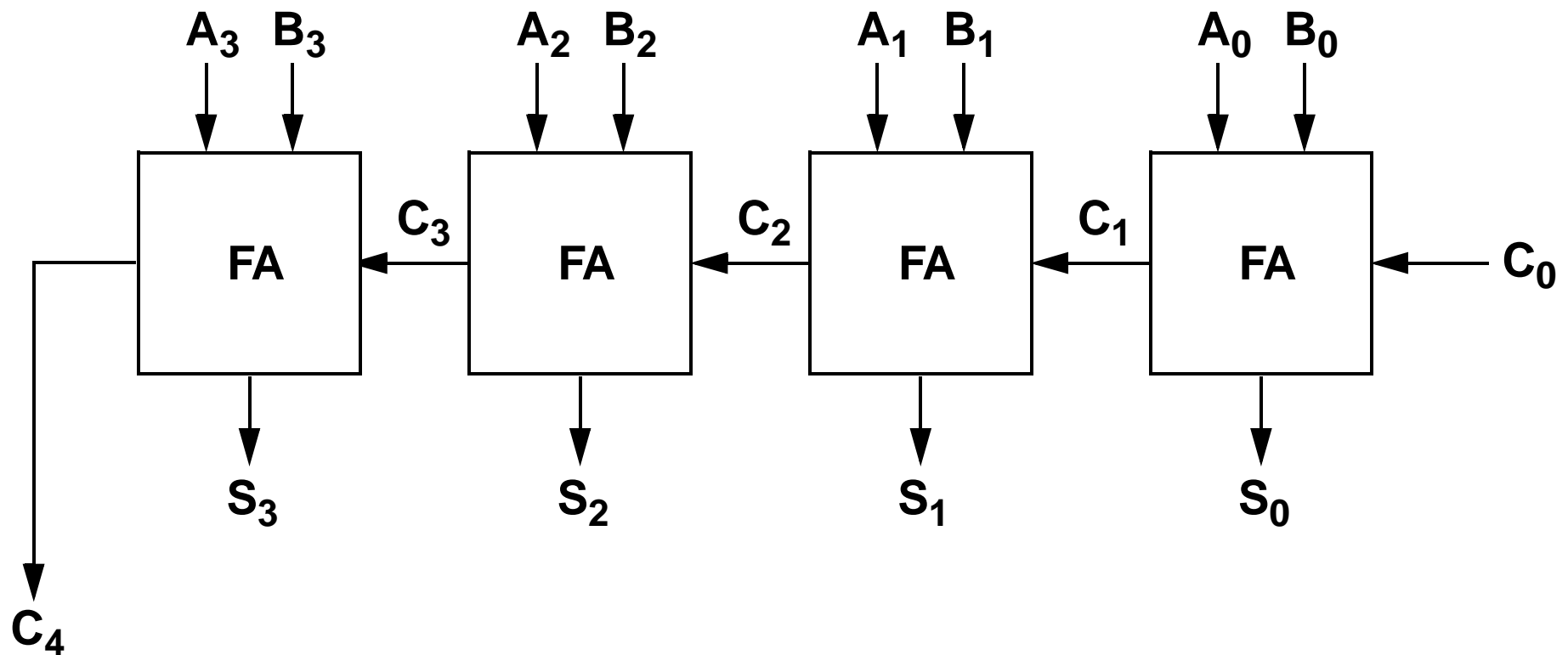
- A 4-bit binary adder can be formed with four full-adders as follows.



COMPARATORS

MAGNITUDE COMPARATOR

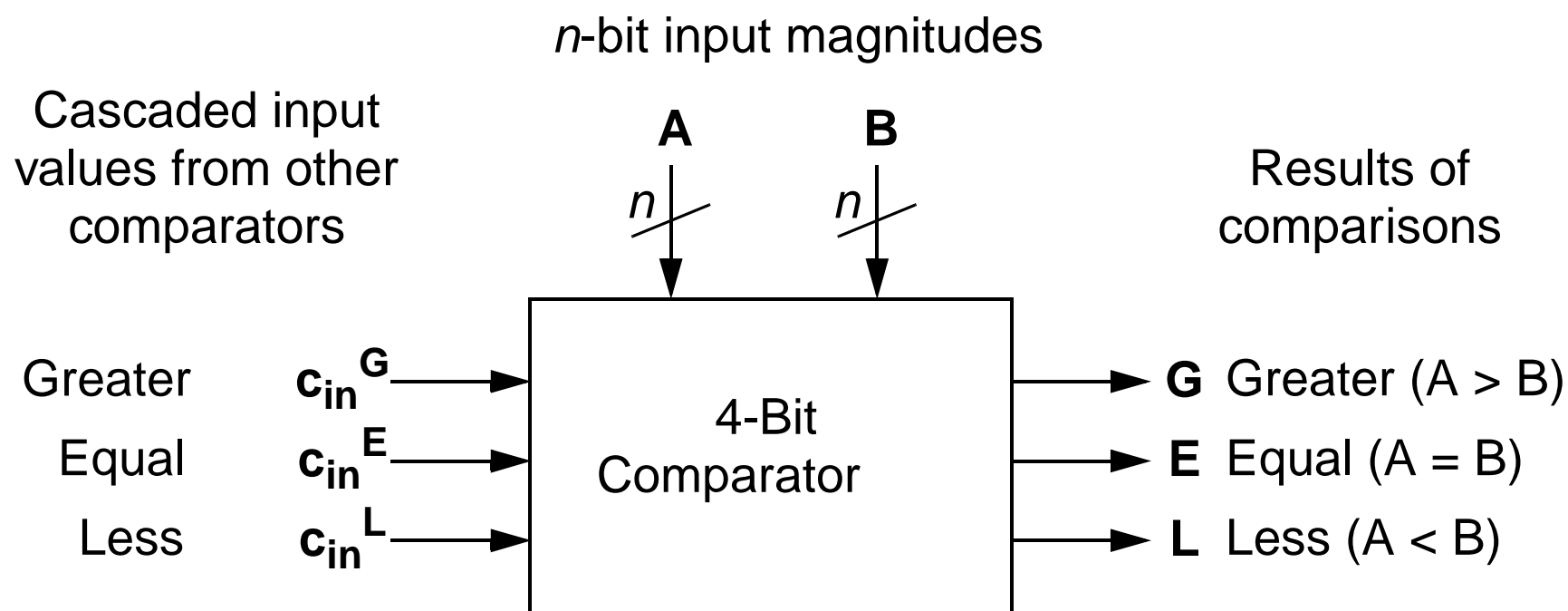- Given two n -bit magnitudes, A and B, a comparator indicates whether
 - $A = B$, $A > B$, or $A < B$



COMPARATORS

MAGNITUDE COMPARATOR

- The approach is to use the XNOR function (equivalence) on each of the n -bits as follows

$$x_i = \mathbf{A_iB_i} + \overline{\mathbf{A_iB_i}} = \overline{\mathbf{A_i} \oplus \mathbf{B_i}}$$

- The Boolean functions for a 4-bit magnitude comparator is as follows
 - $(\mathbf{A} = \mathbf{B}) = x_3x_2x_1x_0$
 - $(\mathbf{A} > \mathbf{B}) = \mathbf{A_3}\overline{\mathbf{B_3}} + x_3\mathbf{A_2}\overline{\mathbf{B_2}} + x_3x_2\mathbf{A_1}\overline{\mathbf{B_1}} + x_3x_2x_1\mathbf{A_0}\overline{\mathbf{B_0}}$
 - $(\mathbf{A} < \mathbf{B}) = \overline{\mathbf{A_3}}\mathbf{B_3} + x_3\overline{\mathbf{A_2}}\mathbf{B_2} + x_3x_2\overline{\mathbf{A_1}}\mathbf{B_1} + x_3x_2x_1\overline{\mathbf{A_0}}\mathbf{B_0}$

Note: $\mathbf{A_i}\overline{\mathbf{B_i}}$ indicates whether $\mathbf{A_i} > \mathbf{B_i}$, $\overline{\mathbf{A_i}}\mathbf{B_i}$ indicates whether $\mathbf{A_i} < \mathbf{B_i}$, and x_i indicates whether $\mathbf{A_i} = \mathbf{B_i}$.