

# **CHAPTER IX**

## **REGISTER BLOCKS**

### **COUNTERS, SHIFT, AND ROTATE REGISTERS**

READ PAGES 249-275 FROM MANO AND KIME


- Like combinational building blocks, we can also develop some simple building blocks using registers. These include:
  - Shift registers
  - Rotate registers
  - Counters
- Implementations of these components can use state machines, but, it is often easier to think of them without the complication of a state machine.

# SHIFT REGISTERS


## INTRODUCTION

- Logical shift registers take the bits stored and move them up a significant bit or down a significant bit.


### LOGICAL SHIFT RIGHT (LSR)

 


### ARITHMETIC SHIFT RIGHT (ASR)

 

### LOGICAL SHIFT LEFT (LSL)

 

### ARITHMETIC SHIFT LEFT (ASL)

 


- Notice that logical and arithmetic shift lefts are the same.

# SHIFT REGISTERS
 
## LSR SAMPLE

- A simple implementation of a logical right shift register might look like the following.






# SHIFT REGISTERS
 
## 4-BIT BIDIRECTIONAL


- The following is a 4-bit bidirectional shift register with parallel load.



# SHIFT REGISTERS
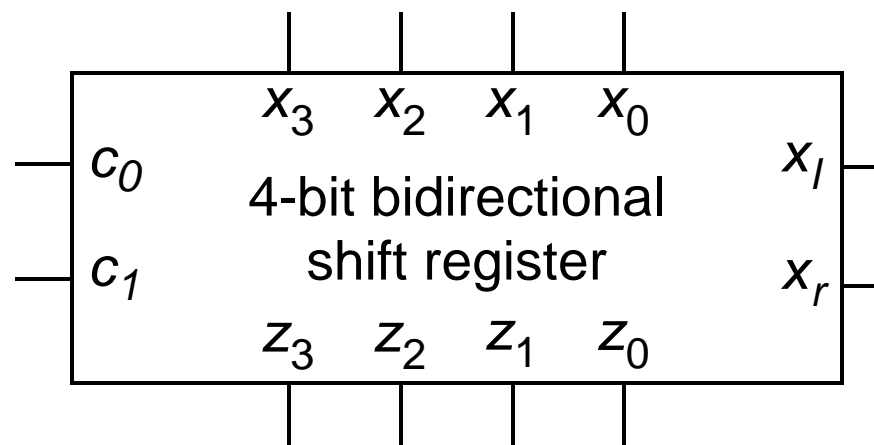
## CASCADING (1)


- Cascading of shift registers can also be done if the discarded bit is used to shift into another shift register module.
- For instance, the 4-bit bidirectional shift register previously presented can be easily cascaded using the
  - $x_r$  (right shift data input) and
  - $x_l$  (left shift data input)



# SHIFT REGISTERS
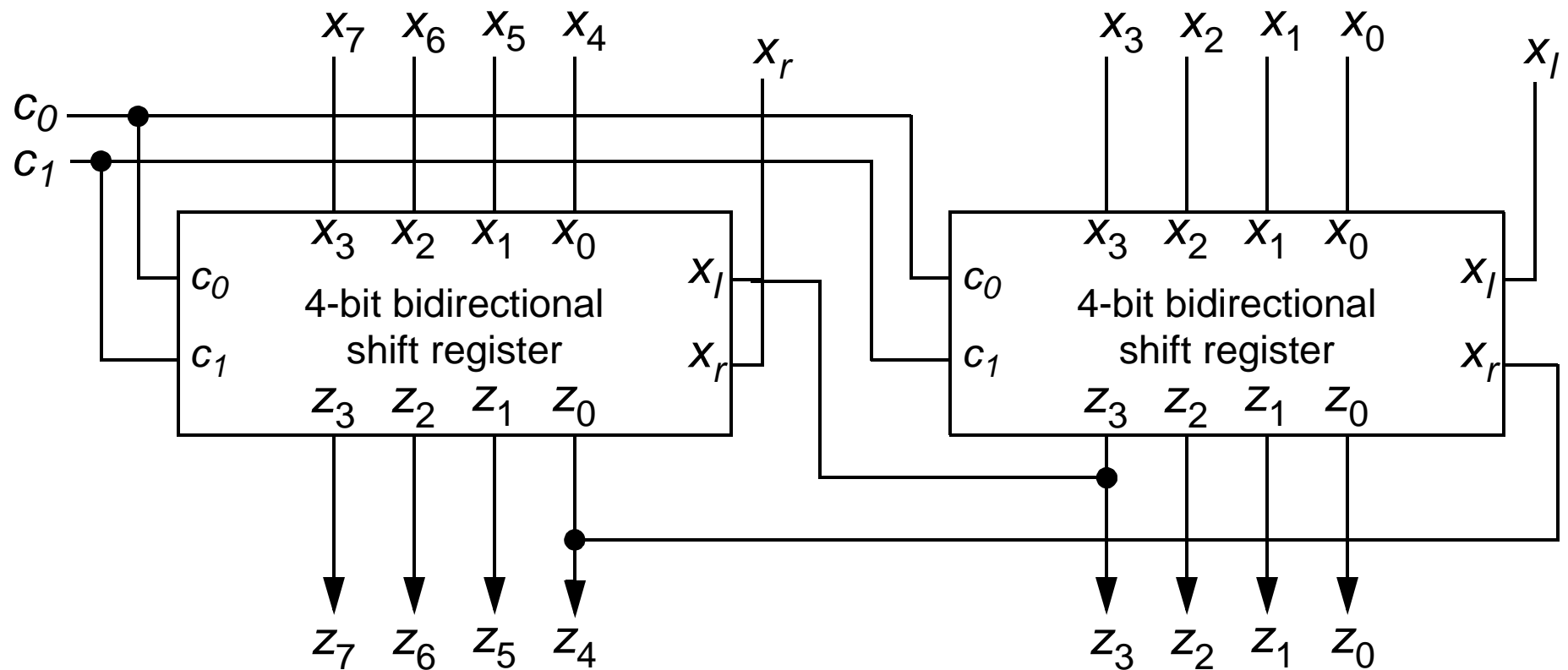
## CASCADING (2)

- For example, an 8-bit bidirectional shift register with parallel load can be formed as follows.






# **ROTATE REGISTERS**


## **INTRODUCTION**

- A rotate register is the same as a logical shift register except that the discarded bit is fed back into the empty space from the shift.


**ROTATE RIGHT**

 


**ROTATE RIGHT WITH CARRY**

 

**ROTATE LEFT**

 


**ROTATE LEFT WITH CARRY**

 

# ROTATE REGISTERS
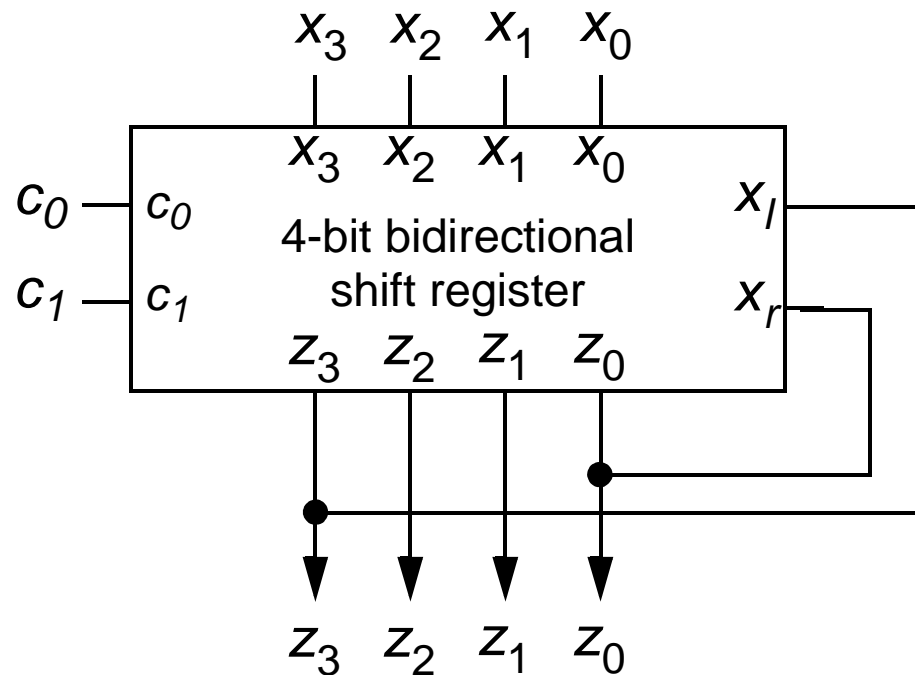
## USING SHIFT REGISTERS

- Rotate registers can actually be implemented using shift registers that have serial data inputs (such as the 4-bit bidirectional shift register discussed).
- For example, a 4-bit rotate register can be formed as follows.



- A counter is a register that on each clock pulse counts up or down, usually in binary.
- Types of counters
  - ripple counters
  - synchronous counters
  - binary counters
  - BCD counters
  - Gray-code counters
  - Ring counters (a 1 moves in a ring from one flip-flop to the next)
  - up/down counters (ability to increment or decrement)
  - counters with a parallel load (load in starting value with parallel input)


# COUNTERS

## MODULO- $P$ COUNTERS

- A modulo- $p$  counter is defined by the following equation.

$$S(t+1) = (S(t) + x) \bmod p$$

 - The state diagram for the modulo- $p$  counter is as follows.




- An  $n$ -bit binary counter consists of  $n$  flip-flops and can count in binary from 0 through  $2^n - 1$ .
- This can be formed with a modulo- $p$  counter where  $p = 2^n$ .
- Two main categories exist for counters:
  - Ripple counters
    - One flip-flop transition serves to trigger other flip-flops.
    - The clock pulse is usually only sent to the first flip-flop.
    - This requires a memory cell that can complement its value.
    - The JK flip-flop would be one approach (we have not studied this!)
  - Synchronous counters
    - Change of state is determined from the present state.
    - Clock pulse sent to all flip-flops.


# COUNTERS
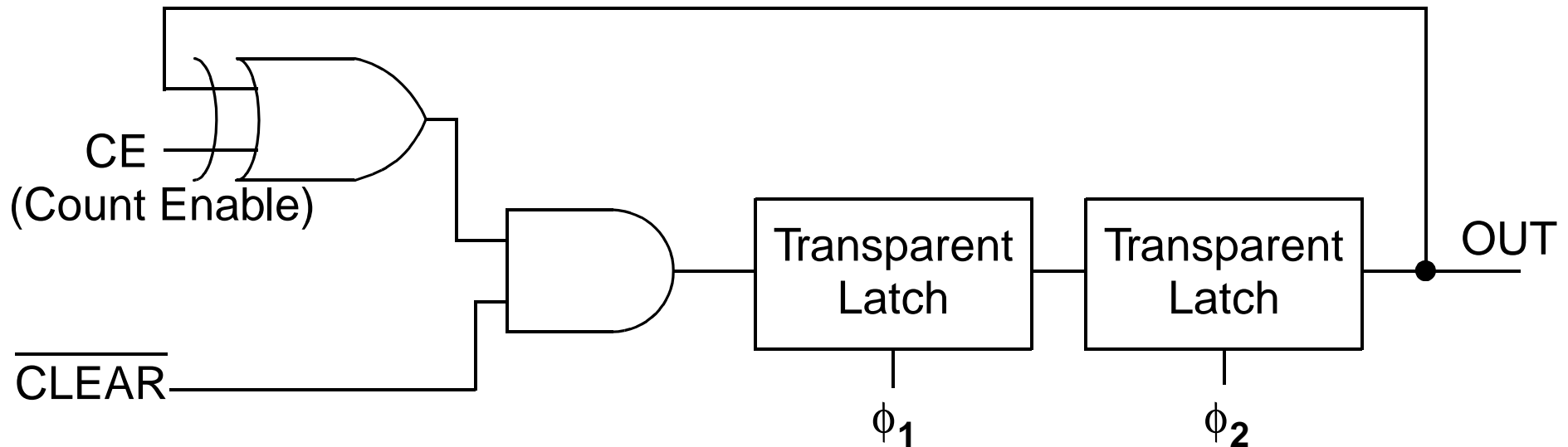
## TOGGLE CELL

- A toggle cell will be useful for implementing counters.




Present Latch Value	CE	$\overline{\text{CLEAR}}$	Next Latch Value	OUT
X	X	0	0	?
0	0	1	0	0
1	0	1	1	1
0	1	1	1	0
1	1	1	0	1

 

# COUNTERS
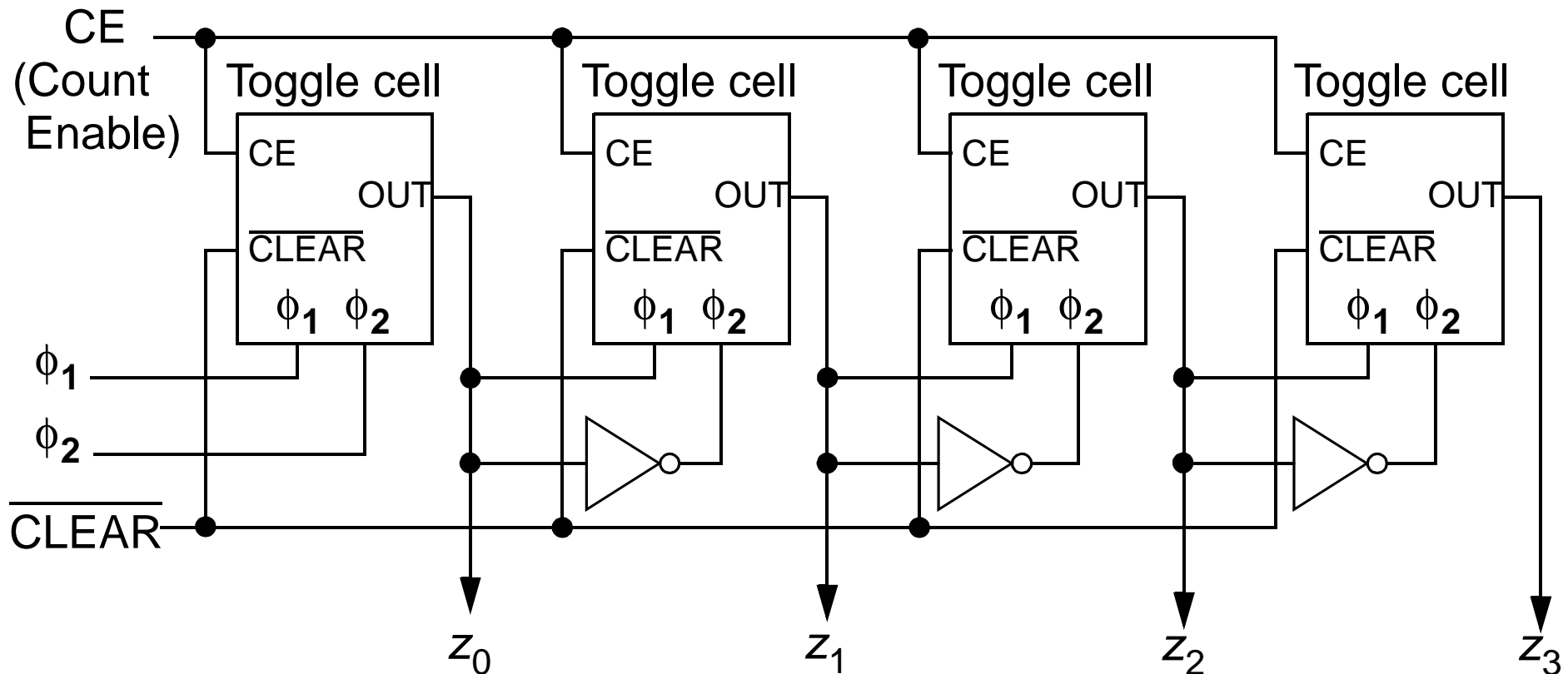
## RIPPLE COUNTER

- The toggle cell can be used as follows to form a ripple counter.




- Notice that the previous toggle cell is connected to the clock input of the next cell. This causes the bits to ripple through the counter.

# COUNTERS
 
## SYNCHRONOUS COUNTER

- Below is an example 4-bit synchronous counter using toggle cells.




- Notice that clock is sent to all toggle cells.
- A simplified form is in Figure 5-11, pp. 269 of Mano & Kime.




# COUNTERS
 
## MORE ON MODULO- $P$

- Notice that the counters developed so far can count from 0 to  $2^n - 1$  for  $n$  toggle cells.
- Therefore, for module- $p$  counting, the  $p$  is currently limited to  $2^n$ .
- How about if we wish  $p$  to be a non-power of 2?
- Need to build what can be referred to as a divide by counter.
- Given the following counter block, a general modulo- $p$  counter can be constructed by clearing the counter after the desired maximum value.



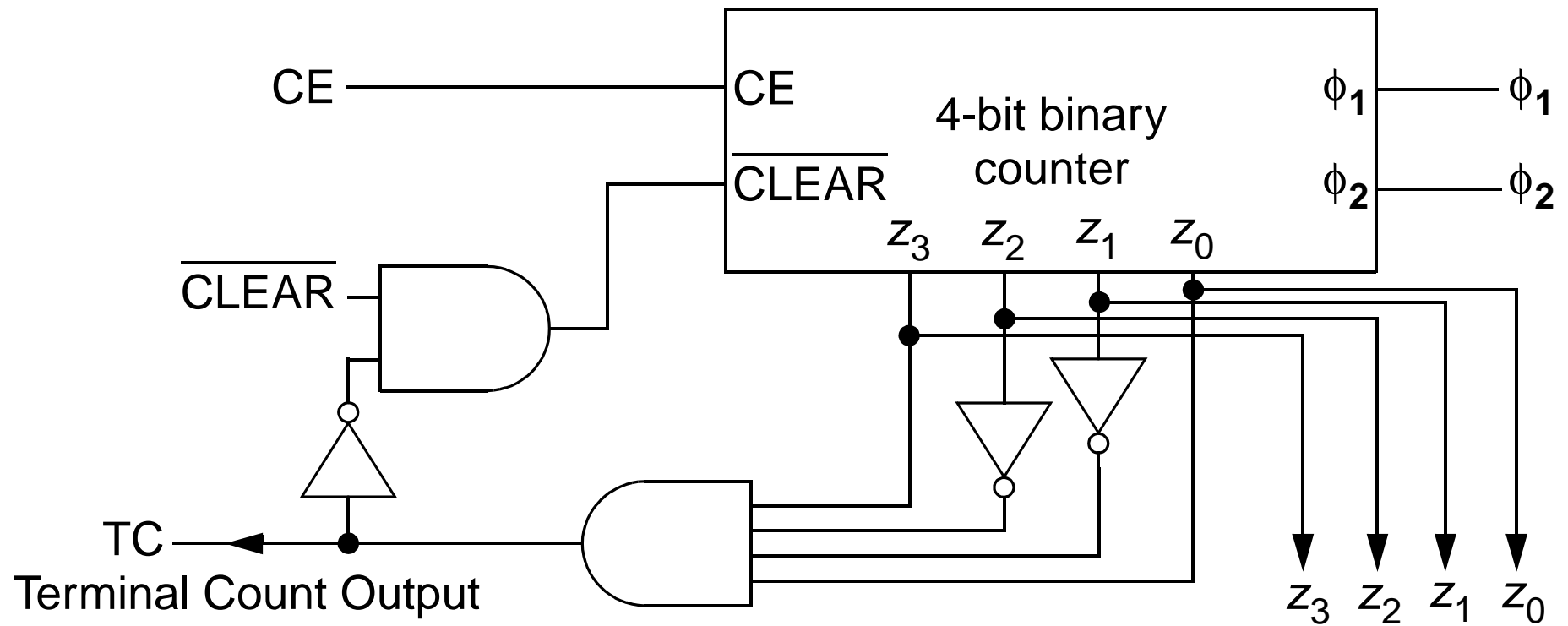


- Notice that the counter is cleared after a value of 9 (**1001**).

# COUNTERS
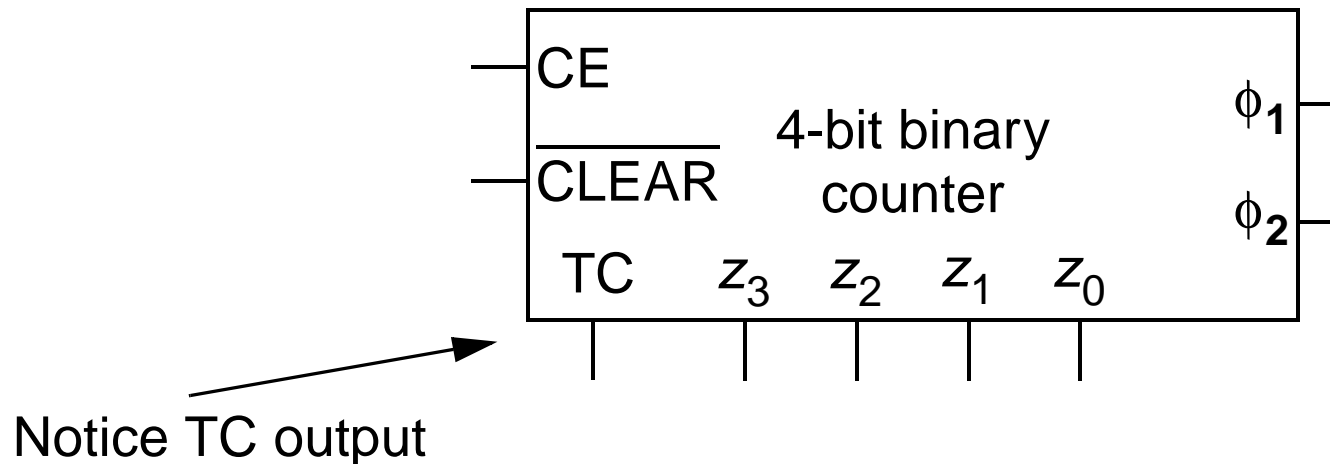
## TERMINAL COUNT (TC)

- The previous BCD counter was built by deriving a terminal count (TC) output signal.
- A terminal count output signal for any counter can be useful, so, we will be included in general block diagram for a binary counter.



- In this 4-bit binary counter example, TC=1 only when the output is **1111**.

# COUNTERS

## CASCADING COUNTERS

- With a terminal count output (TC), counters can be easily cascaded together to form larger counters.
- For instance, an 8-bit binary counter can be formed as follows.

