

CHAPTER XII

SINGLE CYCLE DATAPATH UNIT


READ SINGLE CYCLE DATAPATH FREE-DOC ON COURSE WEBPAGE

SINGLE CYCLE DPU

INCLUDING MEMORY

- SINGLE CYCLE DPU
- ARITHMETIC LOGIC UNIT
- SINGLE CYCLE DPU W/ALU
- IMMEDIATE REGISTER

 - 32x32 bits is not sufficient memory for most computers.
- We can include external memory (SRAM, DRAM, etc.) as follows.



REGISTER FILES

32-BIT WORD, 32 REGISTERS

- For the upcoming datapath designs in the next chapter, we want to have a 32x32 register file with one write input and two read outputs.

X_{ra} - X read address

Y_{ra} - Y read address


Z_{wa} - Z write address

X_{do} - X data out

Y_{do} - Y data out

Z_{di} - Z data in

rwe - register write enable

 


- Note: Two data outputs implemented with two read address decoders.

ADDER/SUBTRACTOR

GENERAL UNIT DIAGRAM

 - An n -bit adder/subtractor unit is often illustrated as follows.



- This unit would have n full-adders internally.

LOGICAL UNIT

INTRODUCTION

- A useful unit would be one that can take two n -bit inputs and perform some logical operation between each of the bits to get an n -bit output.
- For example, given the 8-bit values **0001 1110** and **1001 1000**, we might want to find the **bit-wise logical OR**.

bit-wise	0001 1110
logical OR	1001 1000
	<hr/>
	1001 1110

- Or similarly, the **bit-wise logical AND** of the two 8-bit values.


bit-wise	0001 1110
logical AND	1001 1000
	<hr/>
	0001 1000

- These types of operations are often used for masking and setting bits.

LOGICAL UNIT

GENERAL UNIT DIAGRAM

 - Below is a general unit diagram for an n -bit logical unit.




- Logical operations, such as **AND/OR/NOT/NAND/NOR**/etc., are done for each bit of **A** and **B** to form **F**.

SHIFT UNIT

GENERAL UNIT DIAGRAM

 - Below is a general unit diagram for an n -bit shift unit.




- Notice that the n -bit value **A** will be shifted according to the distance indicated with signed number **B**.

SINGLE CYCLE DPU

ARITHMETIC LOGIC UNIT

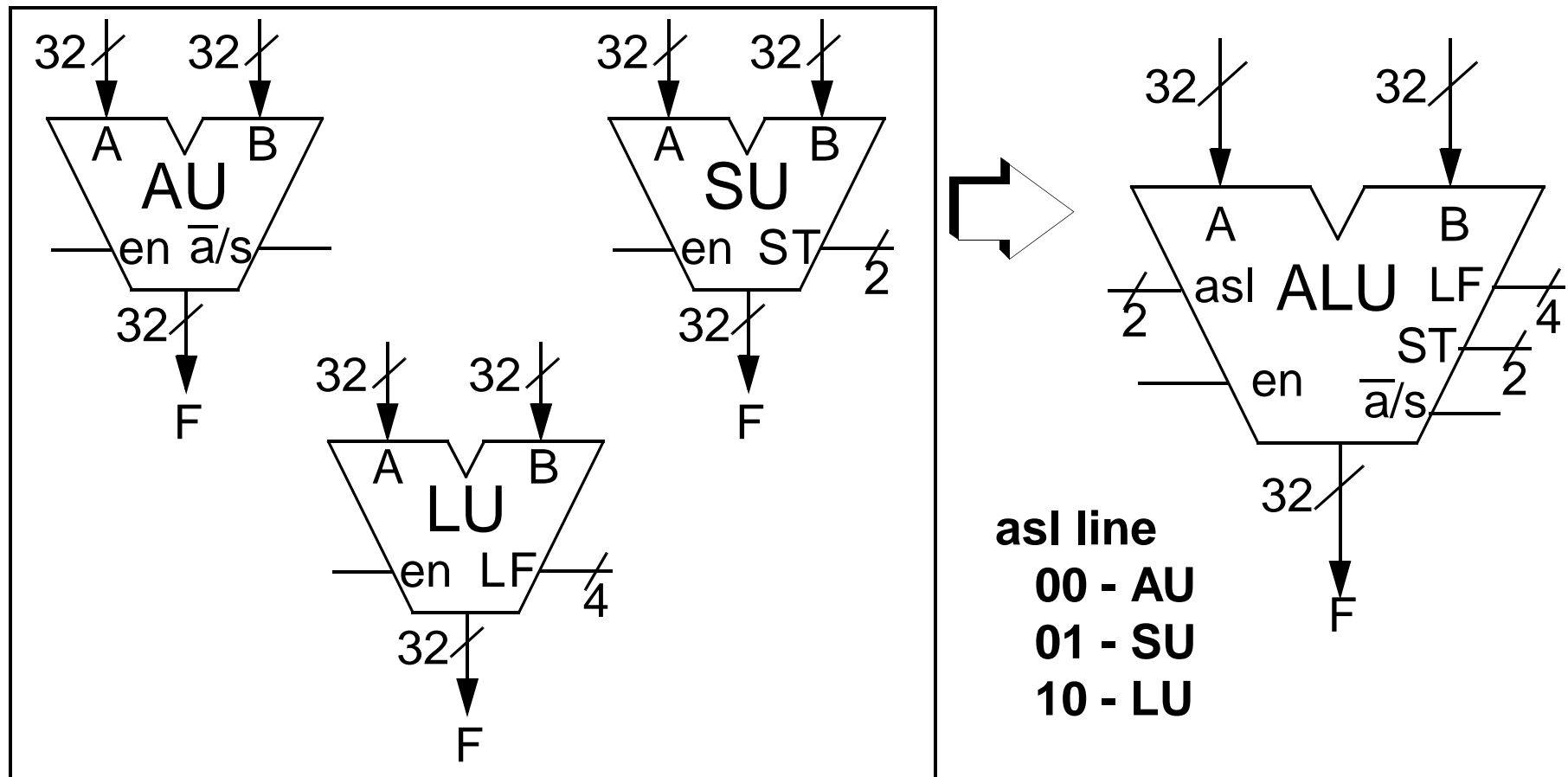
- Since only one of **AU**, **SU**, or **LU** will be active at a time in this architecture, we will combine to form an **arithmetic logic unit (ALU)**.



SINGLE CYCLE DPU

SINGLE CYCLE DPU W/ALU

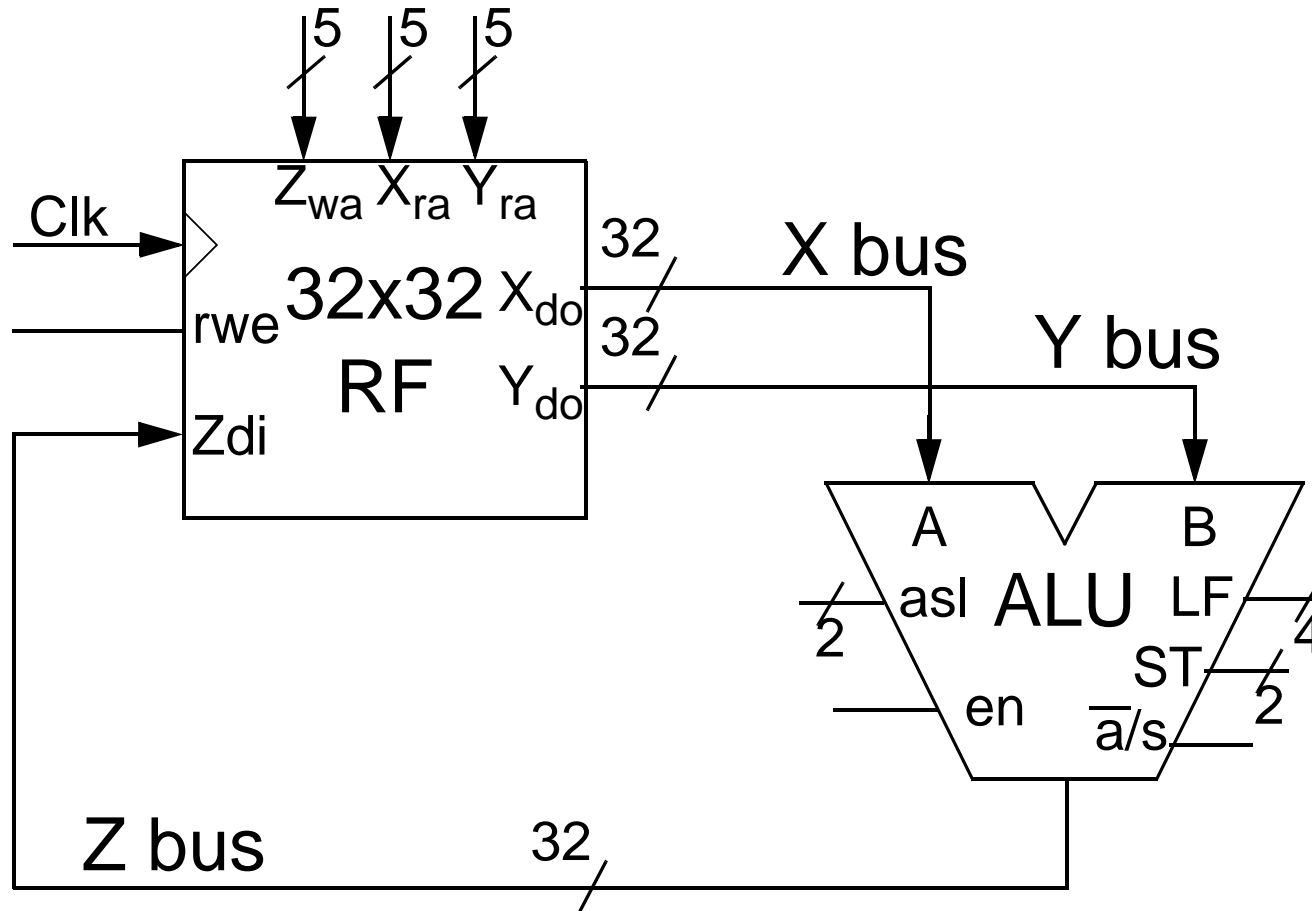- Using our **ALU**, the DPU can be redrawn as follows.



- This structure is still a **triple bus internal DPU architecture**.

SINGLE CYCLE DPU

IMMEDIATE REGISTER

- The **im_en** line does two things:
 - When **0**, **im_en** controls
 - **immediate register outputs** to go to **high impedance** so as **NOT** to affect **Y bus**.
 - **register file Y data out** to output corresponding register value.
 - When **1**, **im_en** controls
 - **immediate register** to output register value to **Y bus**.
 - **register file Y data out** to go to **high impedance** so as **NOT** to affect **Y bus**.
- The **im_va** lines pass a value to the immediate register.

SINGLE CYCLE DPU

MICROCODE

- Microcode in a processor are all of the control signals required to execute an operation for a clock cycle.
- We have actually looked at examples of a microcode operation when we considered various operations such as

$$\mathbf{R3 = R1 + R2}$$

or

$$\mathbf{M[R5] = R9}$$

- Later we will talk about macrocode which are longer operations consisting of many microcode operation over a number of clock cycles.

SINGLE CYCLE DPU

READING FROM MEMORY

- We wish to be able to read and write from our memory.
- A sample read/load operation can be expressed as follows

$$\mathbf{R4 = M[R7]}$$

- This operation uses the value in **R7** as the address to the memory and reads the value at that address in the memory to **R4**.
- What control signals are required?
 - **en = 0** for **ALU**.
 - **X_{ra} = 00111**, **Y_{ra} = XXXXX**, **Z_{wa} = 00100**, and **rwe = 1** for **RF**.
 - **st_en = 0** and **ld_en = 1**
 - **~r/w = r** and **msel = 1**

SINGLE CYCLE DPU


WRITING TO MEMORY

- A sample write/store operation can be expressed as follows


$$\mathbf{M[R5] = R9}$$

- This operation uses the value in **R5** as the address to the memory and write the value in **R9** to that address in the memory.
- What control signals are required?
 - **en = 0** for **ALU**.
 - **X_{ra} = 00101**, **Y_{ra} = 01001**, **Z_{wa} = XXXXX**, and **rwe = 0** for **RF**.
 - **st_en = 1** and **ld_en = 0**
 - **~r/w = w** and **msel = 1**

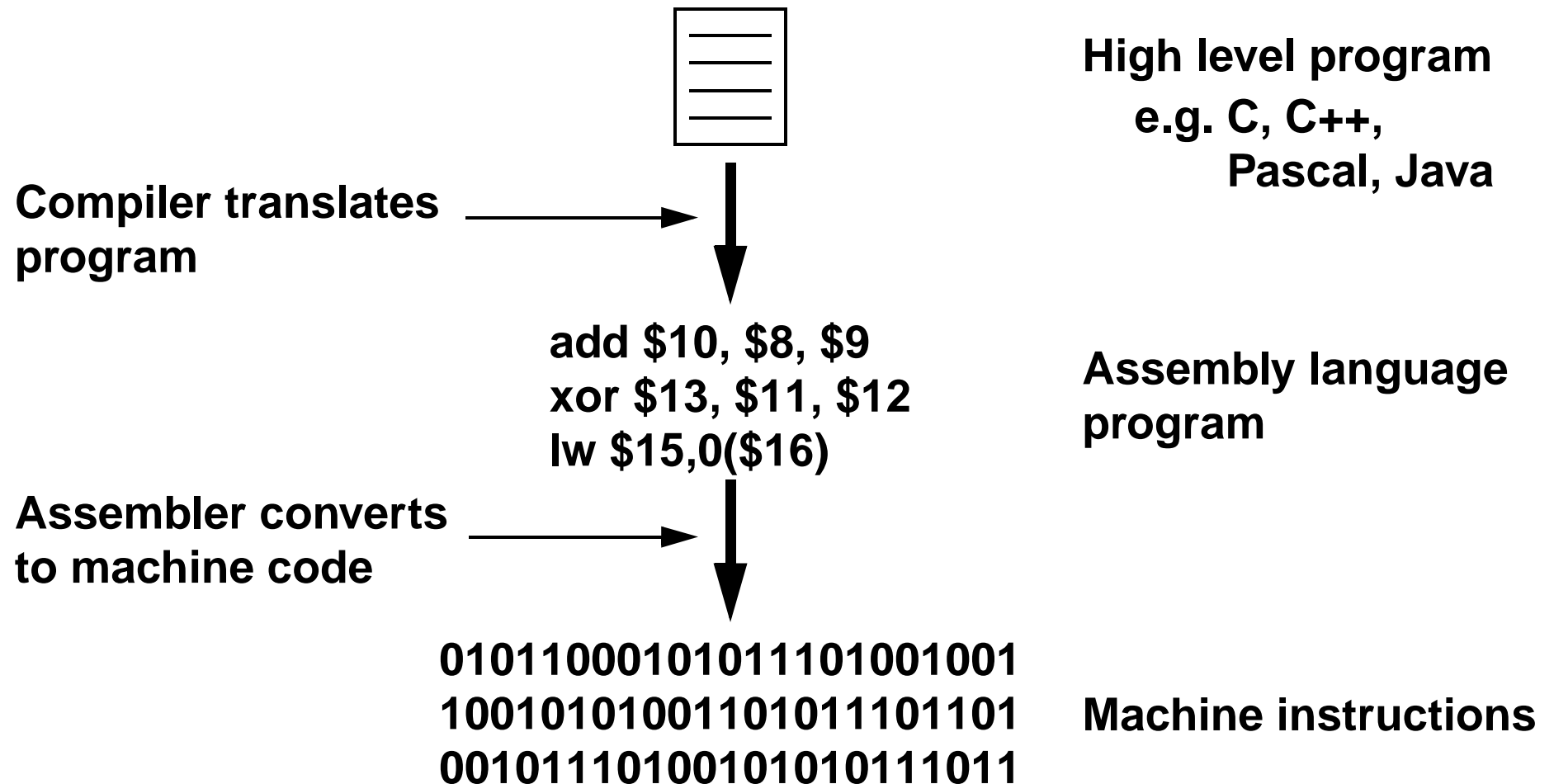- Below is the process for translating a program to machine opcodes.



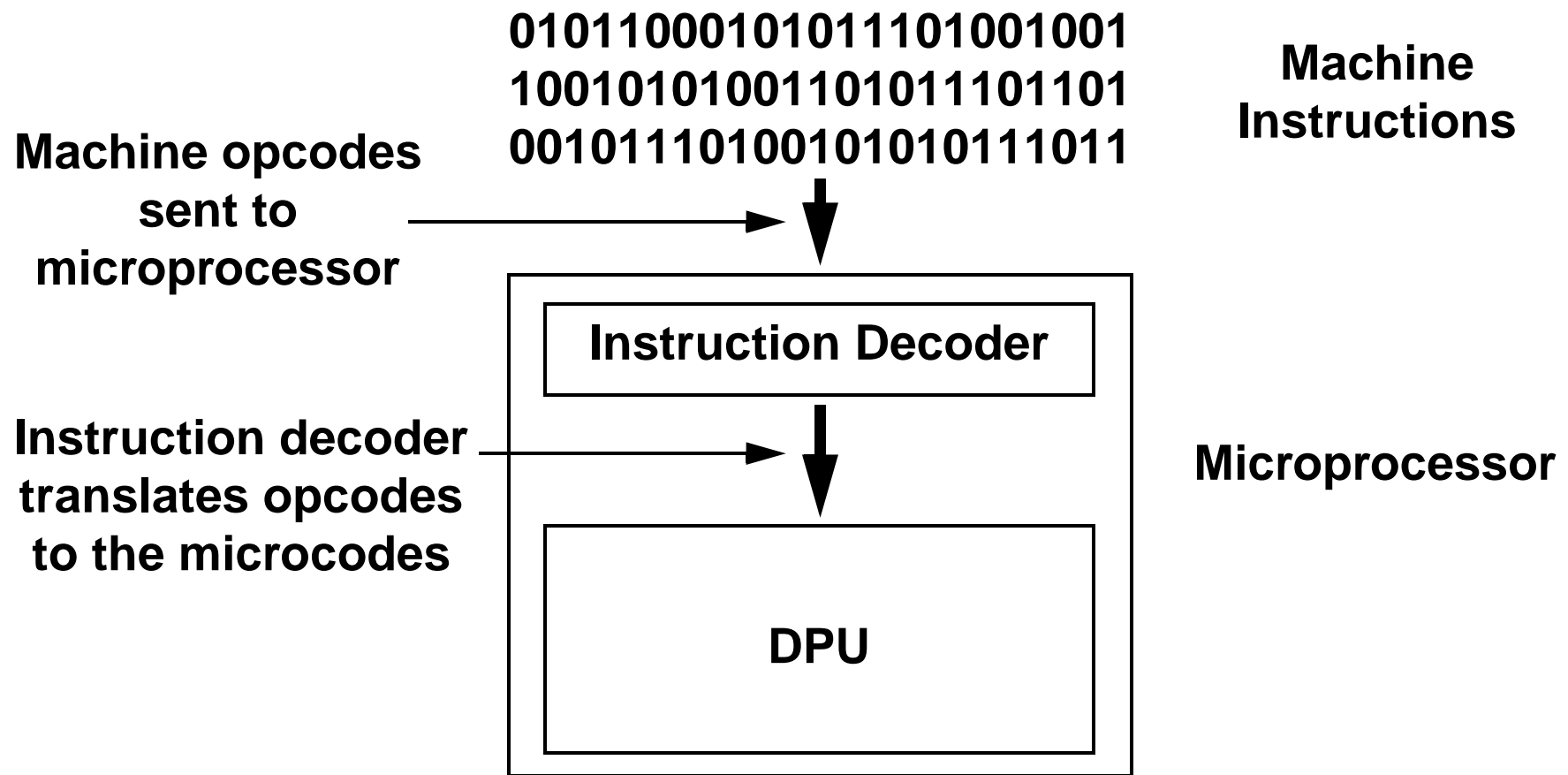- Once the opcodes are given to the microprocessor, it translates the opcode instructions to the microcodes operations we discussed.




INSTRUCTIONS


INSTRUCTION FORMATS

- While instructions can come in many different shapes and forms, we will consider the following 32-bit instruction formats to loosely follow the MIPS R3000/4000 format.

R-format

 


I-format

 

INSTRUCTIONS

INSTRUCTION REGISTER

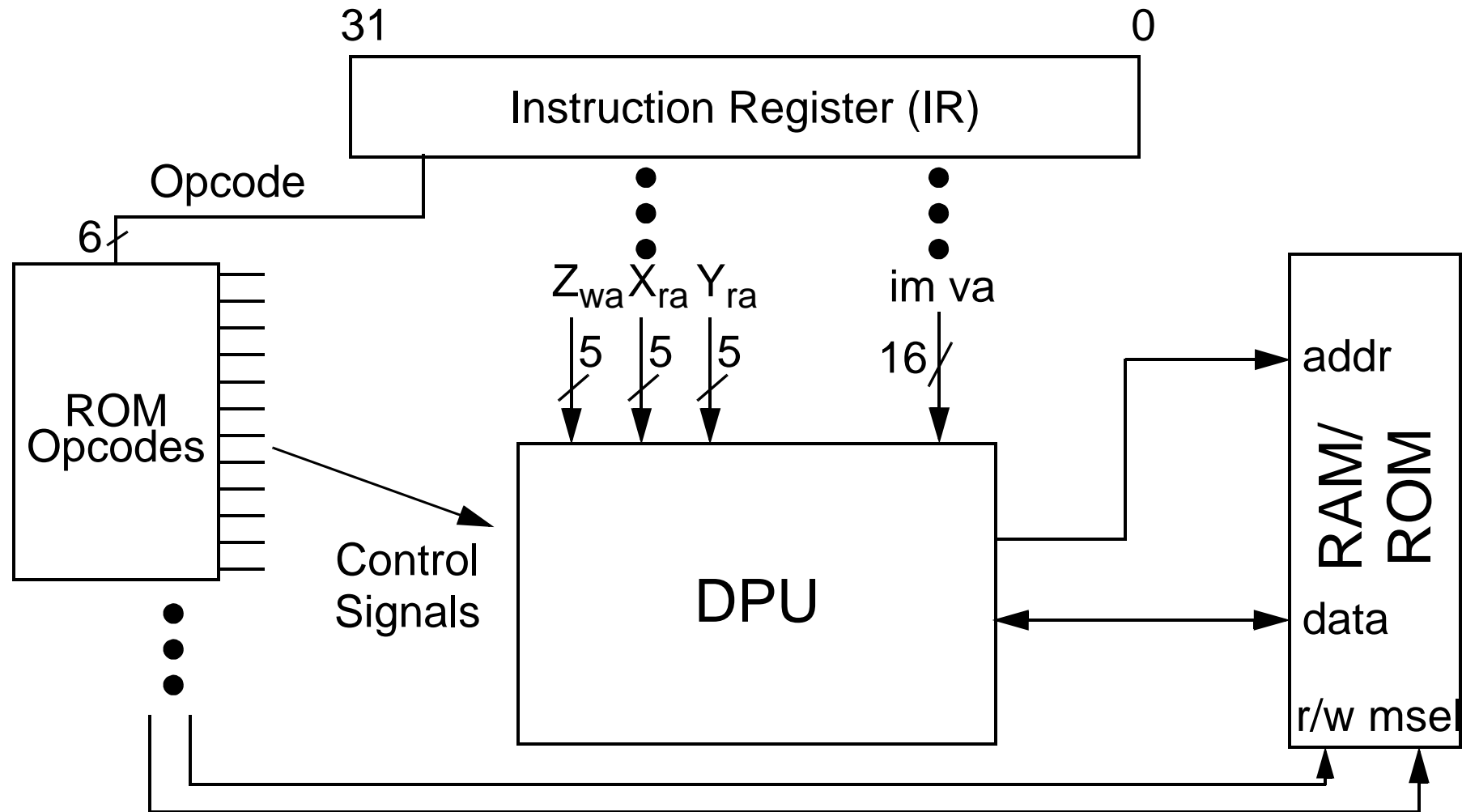
- Use a general instruction register that can act as R- or I-Format.



INSTRUCTIONS

R-FORMAT W/ DPU

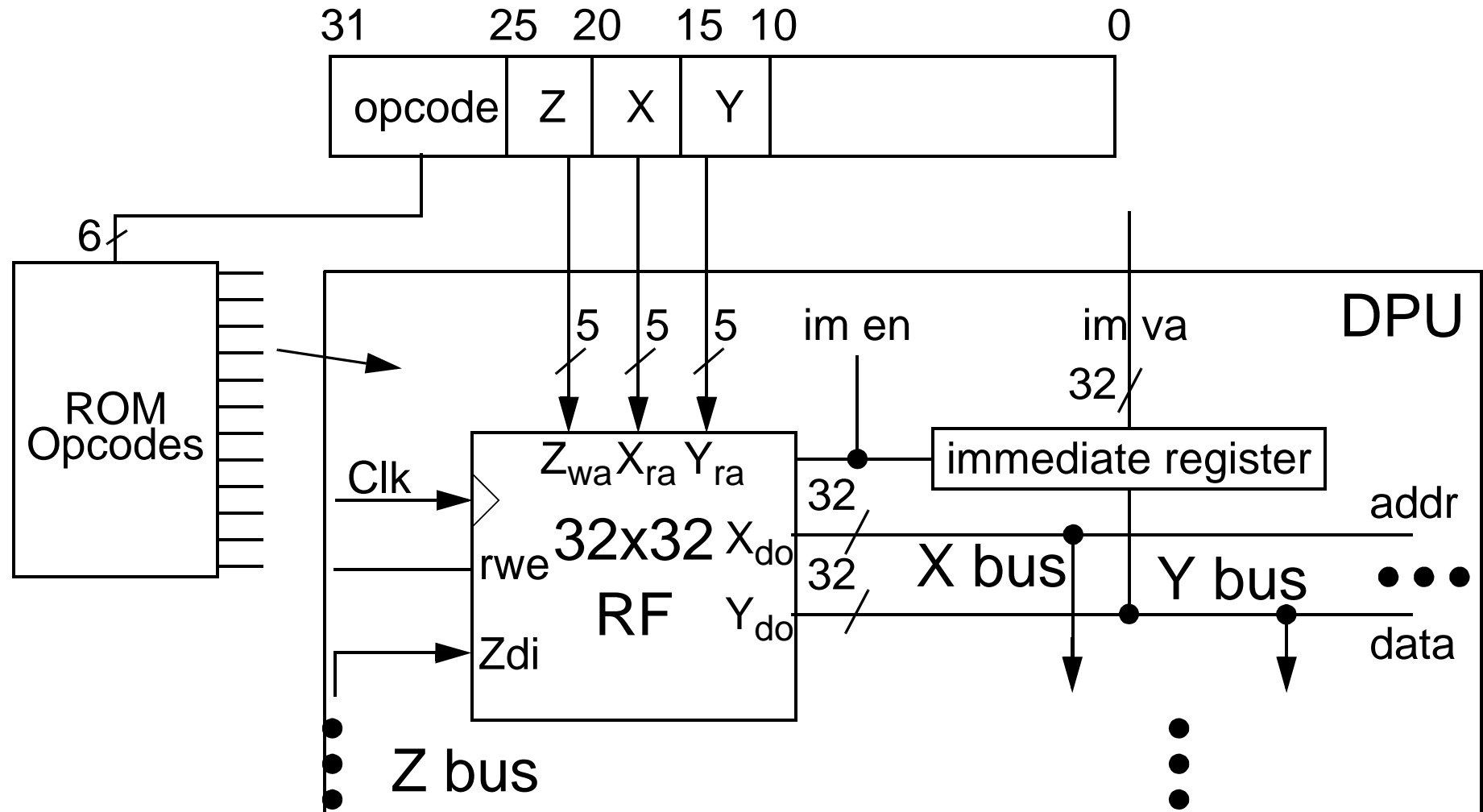- If we have an R-format instruction, we link the bits as follows.



INSTRUCTIONS

I-FORMAT W/ DPU

- If we have an I-format instruction, we link the bits as follows.

